

M. Muradul Bari
Digital Logic Design (2022)
Question Analysis

July - December - 2019


* Simplify the boolean function $F = A'B'C'D + B'CD + A'BCD + AB'C'$ and implement the result using logic gates.

At First I use K-map for simplify.

		CD			
		00	01	11	10
AB	00		1		1
	01				1
	11				
	10	1	1		1

$$F = A\bar{B}\bar{C} + \bar{A}C\bar{D} + \bar{B}C\bar{D} + \bar{B}\bar{C}D$$

resulting logic gates.

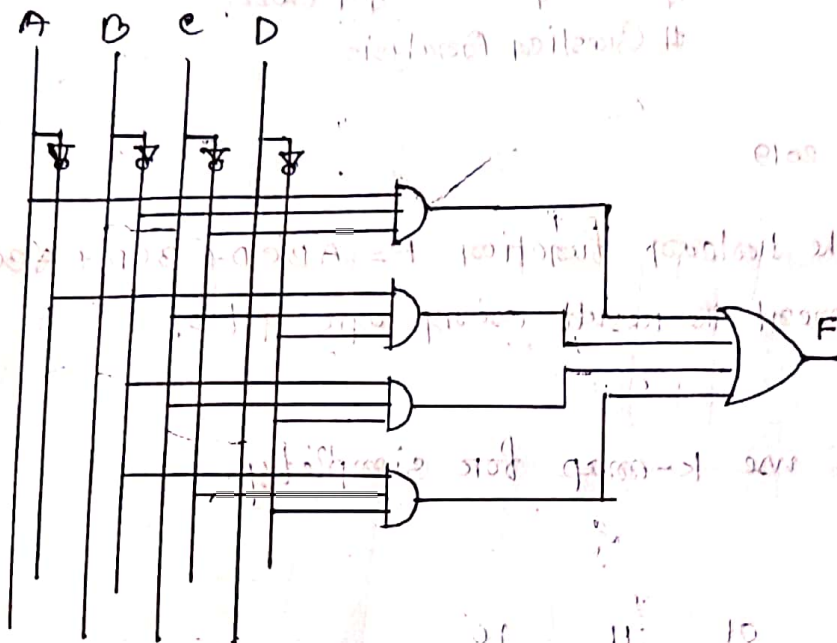


* "An Expression with the minimum number of literals is not necessarily unique" - Illustrate the significance of the above statement with appropriate example:

				11
				11
11		11	11	10

$$A\bar{B}\bar{C} + \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}C = 1$$

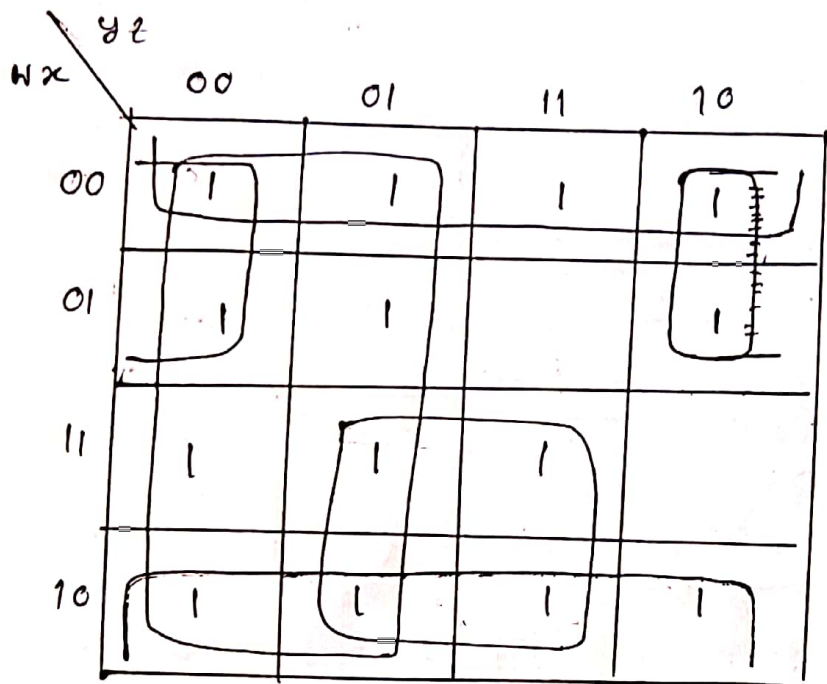* Simplify the boolean function $f(w, x, y, z) = \sum(0, 1, 2, 3, 4, 5, 6, 8, 9, 10, 11, 12, 13, 15)$



$$F = \bar{y} + wz + \bar{x} + \bar{w}x\bar{z}$$

લેખ્યાતી અવજીએ અમણ નિચાલે શલે (K-Map પ્રયોગ)

Since the function has four variable, a four variable map must be used. The minterms listed in the sum are marked by 1, in the map.

* Find the complement of the function $F_1 = xy\bar{z} + \bar{x}\bar{y}z$ and $F_2 = x(y\bar{z} + yz)$ applying De Morgan's theorem.

* Given

$$F_1 = xy\bar{z} + \bar{x}\bar{y}z$$

complements of $\bar{F}_1 = \overline{xy\bar{z} + \bar{x}\bar{y}z}$

$$= \overline{xy\bar{z}} \cdot \overline{\bar{x}\bar{y}z}$$

$$= (\bar{x} + \bar{y} + z)(x + y + \bar{z})$$

$$= (xy + \bar{z}) \cdot (\bar{x}\bar{y} + z)$$

$$= x\bar{y} \cdot \bar{x}\bar{y} \cdot z$$

$$= (\bar{x} + \bar{y})(x + y) \cdot z = (x\bar{y} + \bar{x}y)z$$

distribution

$$\bar{x}(x + y + \bar{z}) + \bar{y}(x + y + \bar{z})$$

$$+ z(x + y + \bar{z})$$

$$\bar{x}x + \bar{x}y + \bar{x}\bar{z} + \bar{y}x + \bar{y}y + \bar{y}\bar{z}$$

$$+ zx + zy + z\bar{z}$$

$$= \boxed{\bar{x}y} + \underline{\bar{x}\bar{z}} + \boxed{\bar{y}x} + \underline{\bar{y}\bar{z}} + \underline{xz}$$

$$\frac{+yz + z}{z}$$

$$\boxed{A + AB = A}$$

Absorption

$$\boxed{\bar{x}y + \bar{y}x + z}$$

	yz	00	01	11	10
x					
0	1				
1					1

$$A + AB \sim$$

$$= \boxed{1 + 1.0}$$

$$= 1 + 0.0$$

$$\boxed{\bar{y} + z + y}$$

* Given:

$$F_2 = x(y\bar{z} + yz)$$

$$F'_2 = \overline{x(y\bar{z} + yz)}$$

$$= \overline{xy\bar{z} + xyz}$$

$$= \overline{xy\bar{z}} \cdot \overline{xyz}$$

$$= (\bar{x} + \bar{y} + z)(\bar{x} + \bar{y} + \bar{z})$$

$$= \bar{x}\bar{x} + \bar{x}\bar{y} + \bar{x}z + \bar{y}\bar{x} + \bar{y}\bar{y} + \bar{y}z + z\bar{y} + \bar{x}\bar{z} + \bar{y}\bar{z} + z\bar{z}$$

$$= \bar{x} + \bar{x}\bar{y} + \bar{x}z + \bar{y}\bar{x} + \bar{y} + \bar{y}z + z\bar{y} + \bar{x}\bar{z} + \bar{y}\bar{z} + 0$$

$$= \bar{x} + \bar{y} + \bar{x}\bar{y} + z\bar{y} + \bar{x}\bar{z} + \bar{y}\bar{z}$$

$$= \bar{x} + \bar{y} + \bar{x}\bar{y} + z\bar{y}$$

$$= \bar{x} + \bar{y}$$

For De Morgan's law:

$$A \cdot \bar{A} = 0 \text{ complement}$$

$$\bar{A} \cdot \bar{A} = \bar{A} \quad \bar{A} \cdot A = 0$$

$$\bar{A} + \bar{A} = \bar{A} \quad A + A = A$$

$$A + AB = A \text{ Absorption}$$


July - December 2017

* Implement the following equations using logic gates.

$$F = x\bar{y}z + \bar{x}y\bar{z} + x\bar{y}$$

$$F = x\bar{y} + xz$$

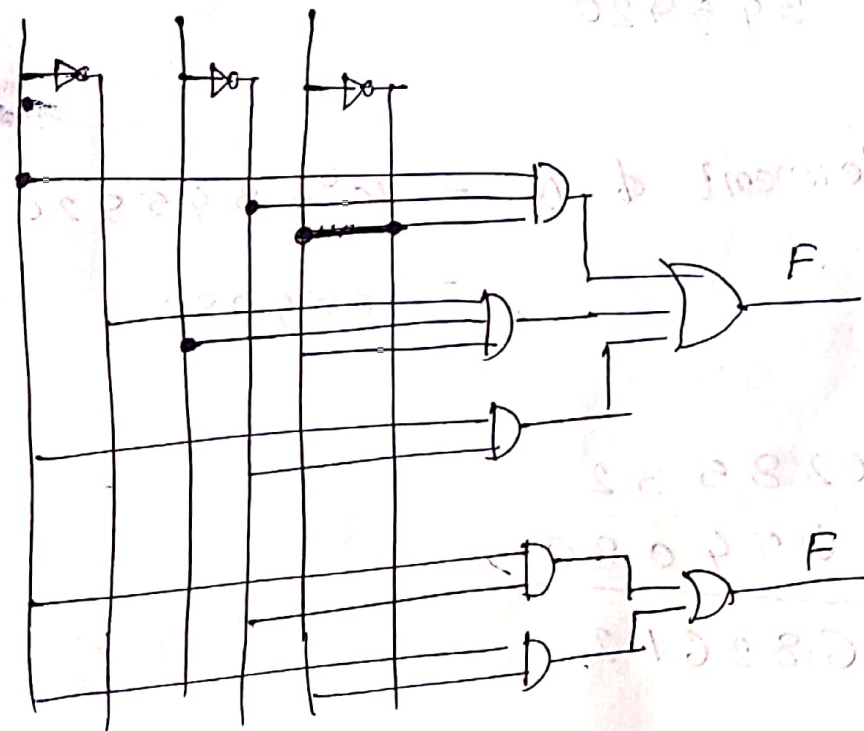Logic Diagram for $F = x\bar{y}z + \bar{x}y\bar{z} + x\bar{y}$



For this logic circuit we use 5 AND (AND) gate and two OR gate. Finally we find the output of function of F.

* Subtract $(28532 - 345920)_{10}$ using
10's complement and $(11010010 - 10001100)_2$
using 1's complement.

$$M = 28532$$

$$N = 345920$$

$$\begin{aligned} \text{10's complement of } N &= 10^6 - 345920 \\ &= 654080 \end{aligned}$$

$$\begin{array}{r} 028532 \\ 654080 \\ \hline \text{No carry} \quad 682612 \end{array}$$

$$\begin{aligned} & - 317388 \\ \text{answer : } & \cancel{+ 682612} = - (\text{10's complement of } 682612) \end{aligned}$$

$$M = 11010010$$

$$N = 10001100$$

1's complement of $N = 01110011$

$$\begin{array}{r}
 11010010 \\
 01110011 \\
 \hline
 \text{Carry } 1 \quad 01000101 \\
 + \quad \quad \quad 1 \\
 \hline
 01000110
 \end{array}$$

answer: 01000110

* Convert $(511.4)_{10}$ to base 5 number

Given number $(511.4)_{10}$

$$\begin{array}{r} \therefore 5 \overline{) 511} \\ 5 \overline{) 102} \rightarrow 1 \\ 5 \overline{) 20} \rightarrow 2 \\ 5 \overline{) 4} \rightarrow 0 \\ 0 - 4 \end{array} \quad \begin{array}{c} \uparrow \\ 1110 \end{array}$$

$$(511)_{10} = (4021)_5$$

$$\begin{array}{r} .4 \\ \times 5 \\ \hline 2.0 \end{array}$$

$$(.4)_{10} = (.2)_5$$

$$\therefore (511.4)_{10} = (4021.2)_5$$

* Prove that $f_1 = m_0 + m_1 + m_5 + m_7 = M_2 \cdot M_3 \cdot M_4 \cdot M_6$

min term				max term		
x	y	z	term	Designation	term	Designation
0	0	0	$\bar{x}\bar{y}\bar{z}$	m_0	$(x+y+z)$	M_0
0	0	1	$\bar{x}\bar{y}z$	m_1	$(x+y+\bar{z})$	M_1
0	1	0	$\bar{x}y\bar{z}$	m_2	$(x+\bar{y}+\bar{z})$	M_2
0	1	1	$\bar{x}yz$	m_3	$(x+\bar{y}+z)$	M_3
1	0	0	$x\bar{y}\bar{z}$	m_4	$(\bar{x}+y+\bar{z})$	M_4
1	0	1	$x\bar{y}z$	m_5	$(\bar{x}+\bar{y}+z)$	M_5
1	1	0	$xy\bar{z}$	m_6	$(\bar{x}+\bar{y}+\bar{z})$	M_6
1	1	1	xyz	m_7		m_7

$$f_1 = m_0 + m_1 + m_5 + m_7$$

$$= \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + x\bar{y}z + xyz$$

x	y	z	f_1	f_1'
0	0	0	1	0
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	0

complement $f_1' = \bar{x}y\bar{z} + x\bar{y}\bar{z} + x\bar{y}z + xyz$

$$= (x+\bar{y}+z)(x+\bar{y}+\bar{z})(\bar{x}+y+z)(\bar{x}+\bar{y}+z)$$

$$= M_2 M_3 M_4 M_6$$

* What are the advantages and disadvantages of digital technique over analog technique.

Advantages of digital technique


1. Digital circuit are more reliable
2. Easy to design
3. cheaper than analog circuit
4. Information stored is easy
5. Accuracy and precision are greater
- 6.

disadvantages of digital technique

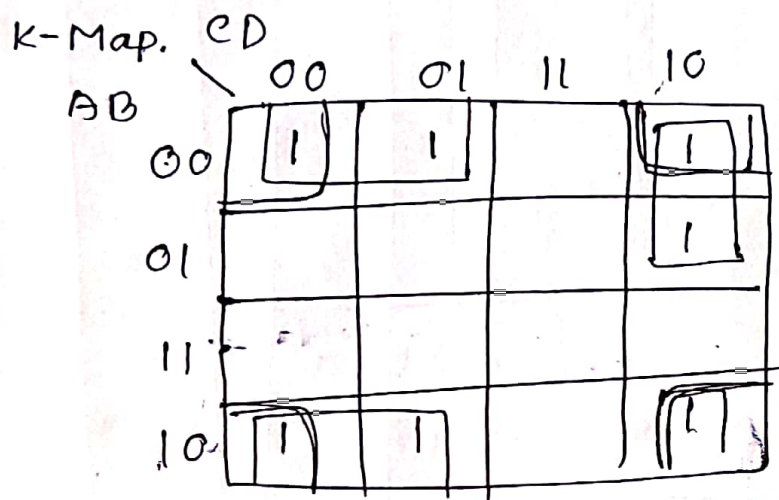1. less data security
2. more complexity
3. Work overload
4. plagiarism and copyright
5. Digital Media Manipulation


* Simplify the boolean function and implement the result using logic gates. $F = \bar{A}\bar{B}\bar{C} + \bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + A\bar{B}\bar{C}$.

The function have four variable. so we use a four variable karnaugh map where the minterm listed in the sum are marked by 1.



$$F = \bar{B}\bar{C} + \bar{A}C\bar{D} + \bar{B}D$$

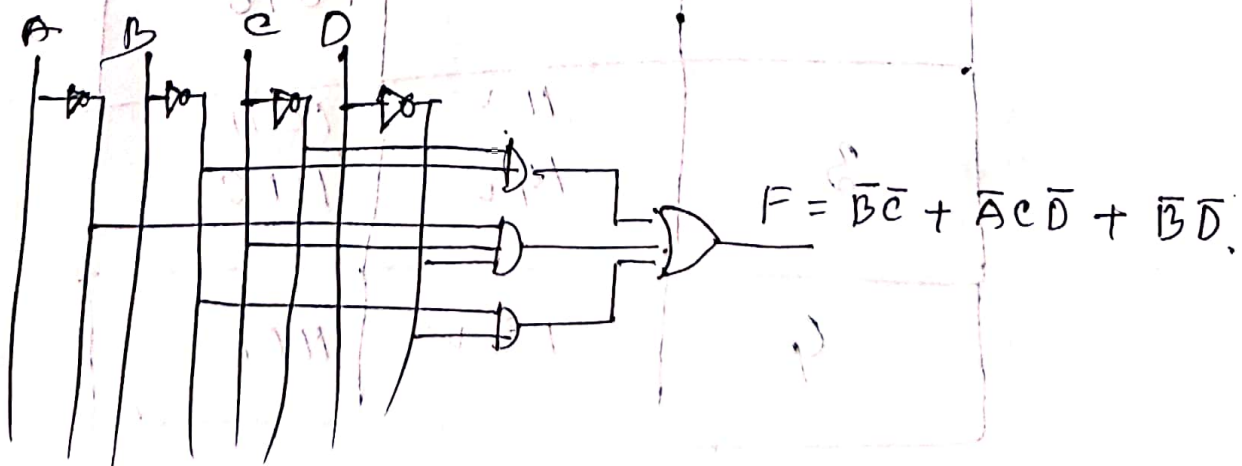Now implement the function $F = \bar{B}\bar{C} + \bar{A}C\bar{D} + \bar{B}D$ using logic gates.



* Me-cluskey method (Tabulation Form).

$$f = (a, b, c, d) = \sum (0, 5, 8, 9, 10, 11, 14, 15)$$

$$0 = 0000$$

$$5 = 0101$$

$$8 = 1000$$

$$9 = 1001$$

$$10 = 1010$$

$$11 = 1011$$

$$14 = 1110$$

$$15 = 1111$$

	00	01	11	10
00	1			1
01	1			
11				
10				1

Step - 01

Group	miniterm	Variable
0	0 ✓	0 0 0 0
1	8 ✓	1 0 0 0
2	5 ✓ 9 ✓ 10 ✓	0 1 0 1 1 0 0 1 1 0 1 0
3	11 ✓ 14 ✓	1 0 1 1 1 1 1 0
4	15 ✓	1 1 1 1

Step 02

Group	matched pair	Variable A B C D
0	0, 8	- 0 0 0
1	8, 9 ✓	1 0 0 -
	8, 10 ✓	1 0 - 0
	9, 11 ✓	1 0 - 1
2	10, 11 ✓	1 0 1 -
	10, 14 ✓	1 - 1 0
3	11, 15 ✓	1 - 1 1
	14, 15 ✓	1 1 1 -

Step 03

Group	match pair	Variable A B C D
0	8, 9, 10, 11	1 0 - -
	8, 10, 9, 11	1 0 - -
1	10, 11, 14, 15	1 - 1 -
	10, 14, 11, 15	1 - 1 -
	0, 8	- 0 0 0
	5	0 1 0 1

} $A\bar{B}$

} AC

Step 04

Prime. Imp.	0	5	8	9	10	11	14	15
8, 9, 10, 11			X	(X)	X	X		
10, 11, 14, 15					X	X	(X)	(X)
0, 8	(X)		X					
5		(X)						

$$= A\bar{B} + A\bar{C} + \bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D$$

3A {

3A {

0 0 0 0	0 0 0 0
0 0 0 1	0 0 0 1
0 0 1 0	0 0 1 0
0 0 1 1	0 0 1 1
0 1 0 0	0 1 0 0
0 1 0 1	0 1 0 1
0 1 1 0	0 1 1 0
0 1 1 1	0 1 1 1
1 0 0 0	1 0 0 0
1 0 0 1	1 0 0 1
1 0 1 0	1 0 1 0
1 0 1 1	1 0 1 1
1 1 0 0	1 1 0 0
1 1 0 1	1 1 0 1
1 1 1 0	1 1 1 0
1 1 1 1	1 1 1 1

* Find prime implicants.

$$F = \sum (0, 1, 2, 8, 10, 11, 14, 15)$$

	0	1	2	8	10	11	14	15
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	0
2	0	0	1	0	0	0	0	0
8	1	0	0	0	0	0	0	0
10	1	0	1	0	0	0	0	0
11	1	0	1	1	0	0	0	0
14	1	1	1	0	0	0	0	0
15	1	1	1	1	0	0	0	0

Step 01

Group	min term	Variable
0	0 ✓	A B C D
1	1 ✓	0 0 0 1
2	2 ✓	0 0 1 0
3	8 ✓	1 0 0 0
4	10 ✓	1 0 1 0
5	11 ✓	1 0 1 1
6	14 ✓	1 1 1 0
7	15 ✓	1 1 1 1

Step 02

Group	matched pair	Variable
0	0, 1	0 0 0 0
	0, 2 ✓	0 0 1 0
	0, 8 ✓	1 0 0 0
1	2, 10 ✓	0 0 1 0
	8, 10 ✓	1 0 1 0
2	10, 11 ✓	1 0 1 1
	10, 14 ✓	1 1 1 0
3	11, 15 ✓	1 1 1 1
	14, 15 ✓	1 1 1 1

Step 03

Group	match pair	varian
0	0, 2, 8, 10	0 0 1 0
	0, 8, 2, 10	0 0 1 0
1	10, 11, 14, 15	1 1 1 1
	10, 14, 11, 15	1 1 1 1
	0, 1	0 0 0 0

B D

A e

step 04

Prime Implicant	0	1	2	3	10	11	14	15
0, 2, 8, 10	X		(X)	(X)	X			
10, 11, 14, 15					X	(X)	(X)	(X)
0, 1	X	(X)						

$$\overline{B}\overline{D} + AC + A\overline{B}\overline{C}$$

$$\frac{1}{2} + \frac{1}{2} =$$

$$\frac{1}{2} \times \frac{1}{2} =$$

$$\frac{1 \times 1}{2} =$$

$$\frac{1}{2}$$

$$1 \times 0 =$$

উদ্দেশ্য হল যে কোন বাইনারি সংখ্যাকে দশমিক-মাত্রা
 দশমিক বাইনারি বাইনারি (দশমিক) আকারে তাকে লিখা দিতে হবে।
 লিখা দিতে হবে যে দশমিক কনভার্স করা তার (যদি) দিতে।
 দশমিক বাইনারি (দশমিক) আকারে তাকে লিখা দিতে হবে
 যেমত দিতে।

$$\begin{array}{r}
 375 \\
 \times 2 \\
 \hline
 0 \mid 750 \\
 \times 2 \\
 \hline
 1 \mid 500 \\
 \times 2 \\
 \hline
 1 \mid 00
 \end{array}$$

$$(0.375)_{10} = (0.11)_2$$

$$\begin{aligned}
 0.11 &= 0 \times 2^{-1} + 1 \times 2^{-2} + 1 \times 2^{-3} \\
 &= \frac{1}{2^2} + \frac{1}{2^3} \\
 &= \frac{1}{4} + \frac{1}{8} \\
 &= \frac{2+1}{8} \\
 &= \frac{3}{8} \\
 &= 0.375
 \end{aligned}$$

Reflected / Gray Code



Reflected	Decimal
0 0 0 0	0
0 0 0 1	1
0 0 1 1	2
0 0 1 0	3
0 1 1 0	4
0 1 1 1	5
0 1 0 1	6
0 1 0 0	7
1 1 0 0	8
1 1 0 1	9
1 1 1 1	10
1 1 1 0	11
1 0 1 0	12
1 0 1 1	13
1 0 0 1	14
1 0 0 0	15